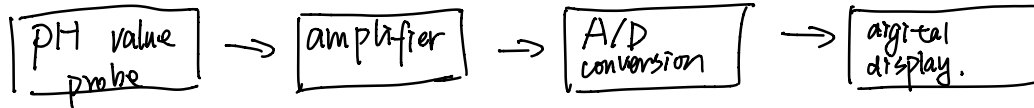



Aim: to measure the pH value of solution and make it stay in an optimum range

System introduction:



1. Measure the pH value.

① Circuit

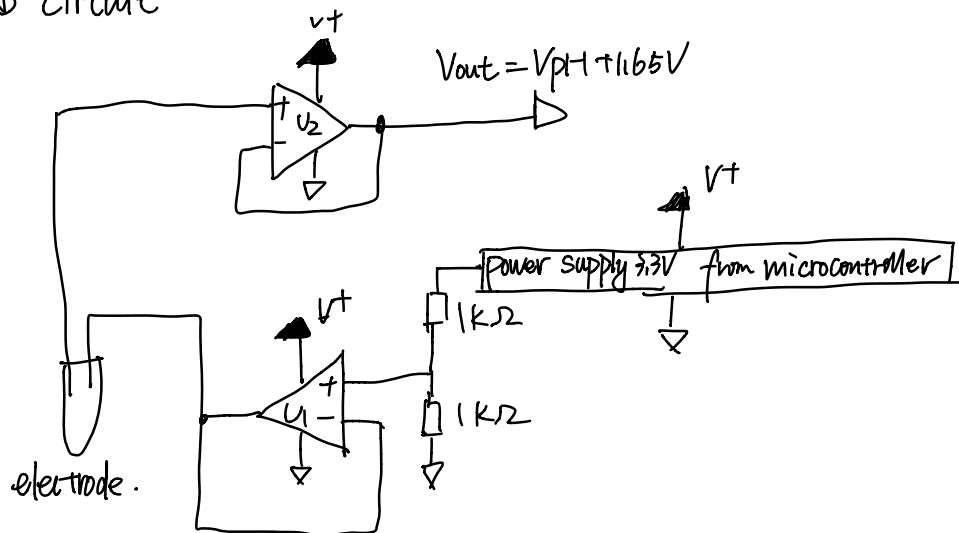

Power supply to op-amp is from microcontroller 5V

$$\text{Potential divider: } \frac{3.3}{2} = 1.65V$$


$U_1$ : adds offset directly to the pH-reference electrode  $\Rightarrow$  stay constant.

(because the pH value sensor has a large Input Impedance).

$U_2$ : adds its individual offset voltage to the output of pH-measuring electrode

(because voltage signal provided by the pH value sensor is too small).

transfer function of pH electrode:

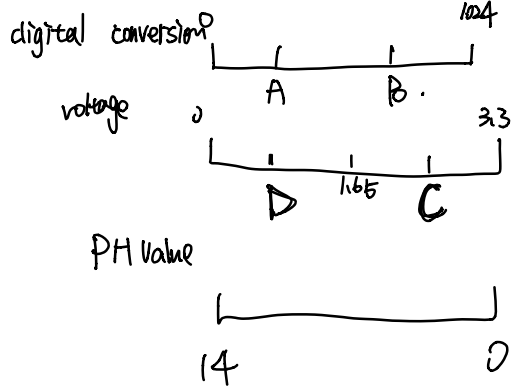

$T$  is temperature of solution in K


$$D = 1.65 - 0.001386T$$

$$C = 1.65 + 0.001386T$$

$$\frac{D-0}{3.3} = \frac{A-0}{1024} \quad A = \frac{1024}{3.3}D$$

$$\frac{C-0}{3.3} = \frac{B-0}{1024} \quad B = \frac{1024}{3.3}C$$

range  $A-B \Rightarrow$  range of pH

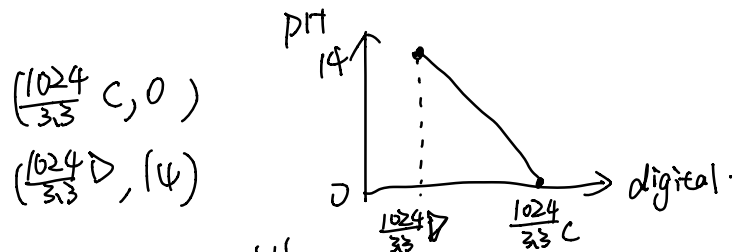

$$y = mx + b$$

$$m = \frac{0-14}{\frac{1024}{3.3}C - \frac{1024}{3.3}D}$$

$$b = -\frac{1024}{3.3}Cm$$

$$y = mx + b \quad y \Rightarrow \text{pH} \quad x \Rightarrow \text{digital}$$

## 2. motor


① If the  $\text{pH} < 4.5$ , pump on. to add base, microcontroller output 5V, transistor 'on' so pump on,

If  $\text{pH} = 5$ , pump stop. microcontroller output 0V.  
transistor 'off', so pump off.

② If the  $\text{pH} > 5.5$ , pump on. to add acid, microcontroller output 5V, transistor 'on' so pump on,

If  $\text{pH} = 5$ , pump stop. microcontroller output 0V.  
transistor 'off', so pump off.

Circuit : transistor = NPN BJT (2N450)

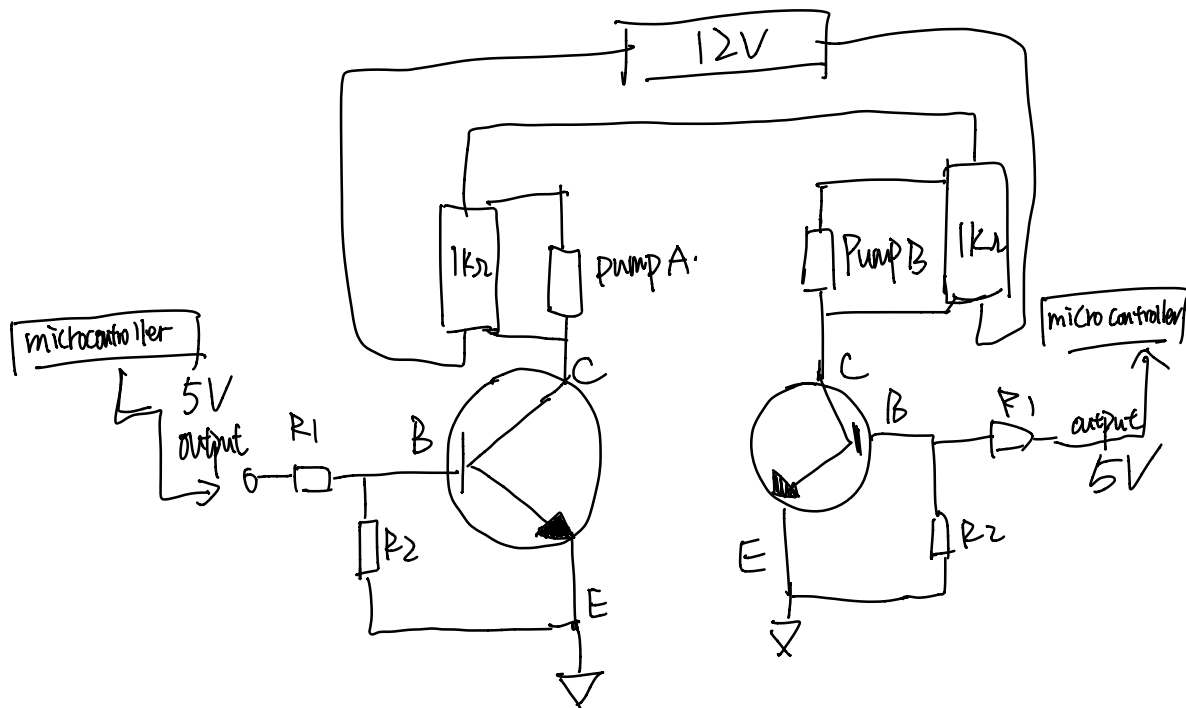

$R_1$  : limit the current.

$R_2$  : prevent the transistor working because of the bias current. (noise).

...  $V_{CC} \times R_2$  ...

$$V_b = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$V_b = 5V$$

$$V_{CC} = 6V$$

$$R_1 = 1k\Omega$$

$$R_2 = 5k\Omega$$